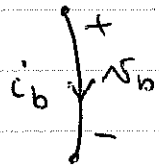


Graph Theoretic Formulation of Network Equations (Vlaek, Singhal, Ch. 3)




v_b is branch voltage
 i_b is branch current

Network is made up of interconnected
branches: b - branches $n+1$ nodes

KVL, KCL are written with respect to the
topology of the network.

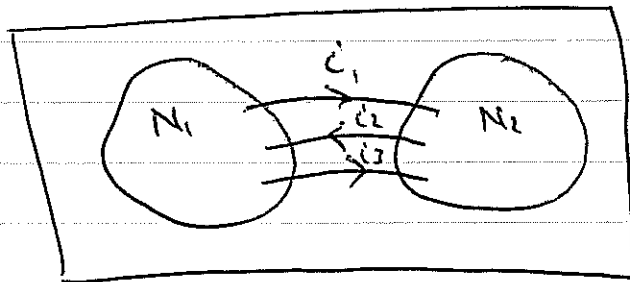If we partition the network into two
sets of nodes:



Generalized KCL says $i_1 + (-i_2) + i_3 = 0$

the partition is called a cut.

KVL: around any closed path the sum of
voltage drops (or increases) is zero.

Note: if we're consistent and always use

i_b as the orientation, then

we could just use v_b and agree that


v_b drops in the direction of the arrow.

This will also give the passive power convention


in which $i_b v_b$ represents the power absorbed

by the branch.

Ex:

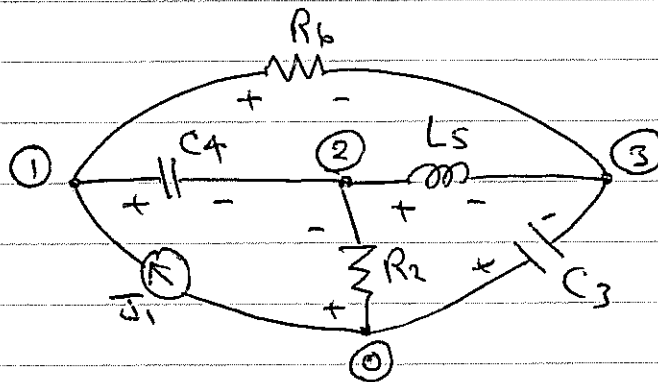

Graph of the network:

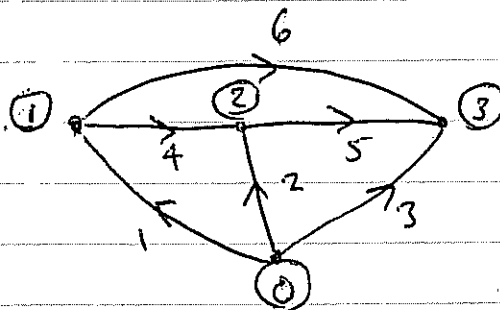

$$n+1 = 4$$

$$b = 6$$

(Node-Edge) Incidence Matrix

$$A \in \mathbb{Z}^{n \times b} \quad A_{ij} = \begin{cases} +1 & \text{if edge } j \text{ leaves node } i \\ -1 & \text{if edge } j \text{ enters node } i \\ 0 & \text{otherwise} \end{cases}$$

For the above example:

$$A = \begin{matrix} & \text{node} & 1 & 2 & 3 & 4 & 5 & 6 \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \begin{bmatrix} -1 & 0 & 0 & 1 & 0 & 1 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 0 & -1 & -1 \end{bmatrix} \end{matrix}$$

Note: node 0 is called the reference node and is not included in A.

It can be shown that $\text{rank } A = n$
i.e., the rows are independent

$$\boxed{\text{KCL: } A \underline{i} = 0}$$

where $\underline{i} = \begin{pmatrix} i_1 \\ \vdots \\ i_b \end{pmatrix}$

Introducing nodal voltages: \underline{v}_n

is vector of branch currents

v_{n1} is the voltage of node ① with respect to the reference node.

The branch voltages can be obtained, for e.g., as


$$v_4 = v_{n1} - v_{n2}$$

or $\underline{v} = A^T \underline{v}_n$ a form of

where $\underline{v} = \begin{pmatrix} v_1 \\ \vdots \\ v_b \end{pmatrix}$ $\underline{v}_n = \begin{pmatrix} v_{n1} \\ \vdots \\ v_{nn} \end{pmatrix}$ KVL.

Cutset and Loopset Matrices

tree:

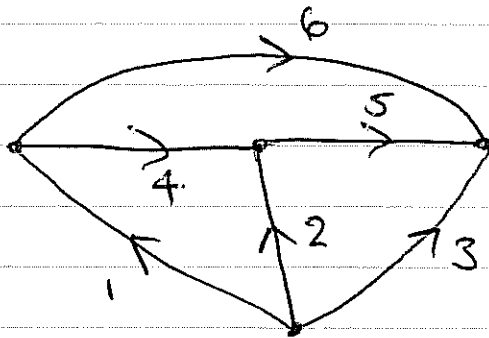


$$n+1 = 4$$

$$b = 6$$

consider the tree made up of branches (edges)

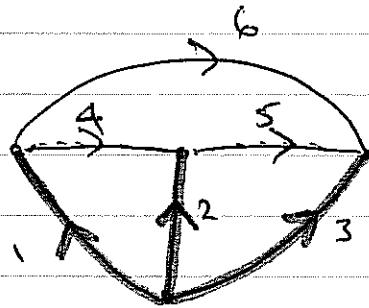1, 2, 3 (called twigs). (a tree will have n branches and no loops).




chords are the remaining branches (edges).

4, 5, 6.


these define the cotree

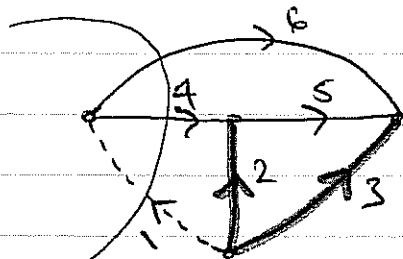if we remove one of the n twigs, we get a partition of nodes of the tree: e.g. remove 1




$$KCL: i_1 - i_4 - i_6 = 0$$

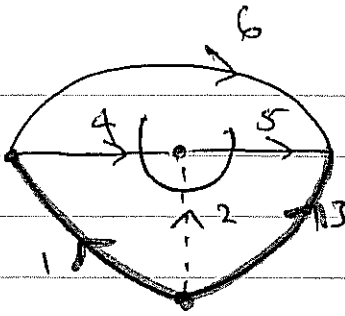basic "cut" defined by removing one twig.



$$\text{KCL: } i_2 + i_4 - i_5 = 0$$

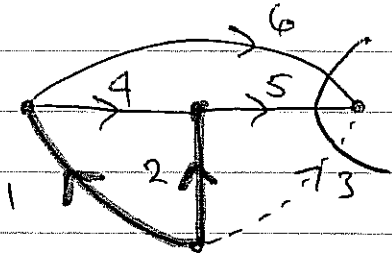

$$\text{KCL: } i_3 + i_5 + i_6 = 0$$

Note: the twig which was removed to define the cut determines the positive direction for the KCL.

The cutset matrix Q :

$$Q = \begin{array}{c} \text{basic} \\ \text{cuts} \end{array} \begin{array}{c} \text{edges} \\ 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \end{array} \begin{array}{c} 1 \\ 2 \\ 3 \end{array} \left[\begin{array}{cccccc|ccc} 1 & 0 & 0 & -1 & 0 & -1 & & & \\ 0 & 1 & 0 & 1 & -1 & 0 & & & \\ 0 & 0 & 1 & 0 & 1 & 1 & & & \end{array} \right]$$

$$Q \underline{i} = 0$$

KCL based on cut


If we number our twigs as $1, \dots, n$

then the form of Q will always be

$$Q = [Q_t \quad Q_c] = [1 \quad Q_c] \quad (n \times b)$$


$$Q_t = 1 \quad n \times n \text{ identity matrix. } -5-$$

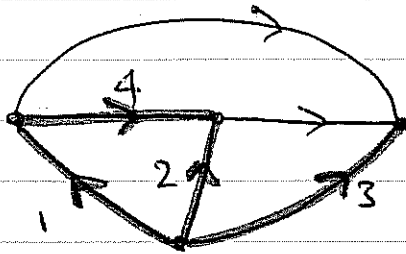Now take the tree and add one chord at a time. (Note there are $b-n$ chords).




this defines a loop for which we can write KVL.

$$\text{KVL: } v_1 - v_2 + v_4 = 0$$

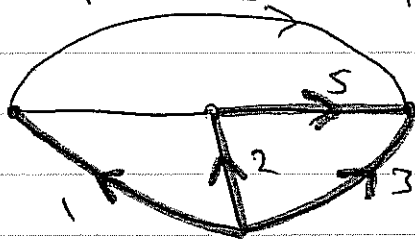

$$\text{KVL: } v_2 - v_3 + v_5 = 0$$

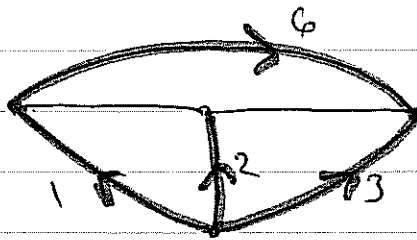

$$\text{KVL: } v_1 - v_3 + v_6 = 0$$

The loopset matrix B :

$$B = \begin{array}{c} \text{loops} \\ \begin{array}{c} 1 \\ 2 \\ 3 \end{array} \end{array} \begin{array}{c} \text{edges} \\ \begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \end{array} \end{array} \begin{bmatrix} 1 & -1 & 0 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 1 & 0 \\ 1 & 0 & -1 & 0 & 0 & 1 \end{bmatrix}$$

$$B = [B_t \ B_c] = [B_t \ I] \quad (b-n) \times b$$

$$B_c = I \quad b-n \times b-n \text{ identity matrix.}$$

It can be shown that

$$\begin{matrix} & B Q^T = 0 & (b-n) \times n \\ \begin{matrix} \nearrow \\ (b-n) \times b \end{matrix} & & \begin{matrix} \nwarrow \\ b \times n \end{matrix} \end{matrix}$$

$$\text{and } \begin{matrix} Q B^T = 0 & n \times (b-n) \\ \begin{matrix} \nearrow \\ (n \times b) \end{matrix} & & \begin{matrix} \nwarrow \\ b \times (b-n) \end{matrix} \end{matrix}$$

i.e.: rows of B are orthogonal to rows of Q

In partitioned form:

$$B Q^T = \begin{bmatrix} B_t & \mathbf{1} \end{bmatrix} \begin{bmatrix} \mathbf{1} \\ Q_c^T \end{bmatrix} = B_t + Q_c^T = 0$$

or $\boxed{B_t = -Q_c^T}$

So B can be written as

$$\boxed{B = \begin{bmatrix} -Q_c^T & \mathbf{1} \end{bmatrix}}$$

$$\boxed{Q = \begin{bmatrix} \mathbf{1} & -B_t^T \end{bmatrix}}$$

Independent Variables

consider the cutset matrix Q_{CL} :

$$Q \underline{i} = 0$$

and partition $\underline{i} = \begin{pmatrix} \underline{i}_t \\ \underline{i}_c \end{pmatrix}$ \underline{i}_t twig currents
 \underline{i}_c chord currents.

$$Q \underline{i} = [1 \quad Q_c] \begin{pmatrix} \underline{i}_t \\ \underline{i}_c \end{pmatrix} = \underline{i}_t + Q_c \underline{i}_c = 0$$

$$\therefore \boxed{\underline{i}_t = -Q_c \underline{i}_c}$$

twig currents
can be obtained
in terms of chord
currents.

$$\therefore \underline{i} = \begin{pmatrix} \underline{i}_t \\ \underline{i}_c \end{pmatrix} = \begin{bmatrix} -Q_c \\ 1 \end{bmatrix} \underline{i}_c = \begin{bmatrix} B_t^T \\ 1 \end{bmatrix} \underline{i}_c$$

$$\boxed{\underline{i} = B^T \underline{i}_c}$$

\therefore chord currents can be considered as
independent variable.

Now consider KVL based on loopset matrix:

$$B \underline{v} = 0$$

$$[B_t \quad \mathbf{1}] \begin{pmatrix} v_t \\ v_c \end{pmatrix} = B_t v_t + v_c = 0 \Rightarrow v_c = -B_t v_t$$

$$\underline{v} = \begin{pmatrix} v_t \\ v_c \end{pmatrix} = \begin{pmatrix} \mathbf{I} \\ -B_t \end{pmatrix} v_t = \begin{pmatrix} \mathbf{1} \\ Q_c^T \end{pmatrix} v_t$$

$$\boxed{\underline{v} = Q_c^T v_t}$$

\therefore twig voltages should be considered as independent variables.

For this reason we should put independent current sources on the cotree and independent voltage sources on the tree



One way to incorporate Sources.
(E.g. of nodal analysis).

- put all independent current sources in cotree. (chords)
- put all independent voltage sources in tree (twigs).

1. start tree by labelling all voltage sources as e_1, \dots, e_l
2. complete tree with remaining passive elements, numbering starting with 1.
3. continue numbering edges of chords starting with passive elements.
4. end with current sources in cotree: j_1, \dots, j_m

Thus, produce the augmented matrix:

Example:

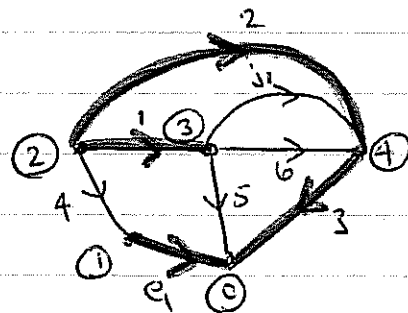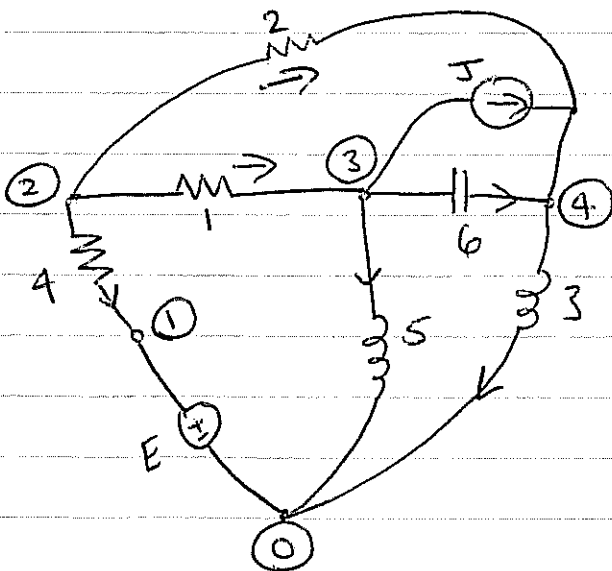

$$A_a = \begin{bmatrix} e_1 & 1 & 2 & 3 & 4 & 5 & 6 & j_1 & \text{node} \\ 1 & 0 & 0 & 0 & -1 & 0 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 & 0 & 0 & 0 & 2 \\ 0 & -1 & 0 & 0 & 0 & 1 & 1 & 1 & 3 \\ 0 & 0 & -1 & 1 & 0 & 0 & -1 & -1 & 4 \end{bmatrix} = [A_e : A : A_j]$$

edges

$$Q_a = \begin{bmatrix} e_1 & 1 & 2 & 3 & 4 & 5 & 6 & i_1 \\ \hline 1 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & -1 & -1 & -1 \\ 0 & 0 & 1 & 0 & 1 & 1 & 1 & 1 \\ 0 & 0 & 0 & 1 & 1 & 1 & 0 & 0 \end{bmatrix}$$

cutset determined by edges
 e_1 }
 1 }
 2 }
 3 }

preserve identity matrix.

Both matrices give us KCL $A_a \underline{i} = 0$
 $Q_a \underline{i} = 0$

For nodal analysis, assume only ind. current sources (if there are voltage sources, assume they can be converted to current src's using Thévenin-Norton $\pm x_r$).

- also assume that every passive element has an admittance constitutive relation:

$$\underline{Y}_b \underline{v}_b = \underline{i}_b$$

$\underline{v}_b, \underline{i}_b$ contain the branch voltages and currents in the passive branches

Then we can use A_a or Q_a as follows:

let $\underline{i} = \begin{pmatrix} \underline{i}_b \\ \underline{j} \end{pmatrix}$ \underline{j} - vector of chord branches with ind. current src's.

$$A_a \underline{i} = 0 \quad (\text{KCL})$$

$$\begin{bmatrix} A & A_j \end{bmatrix} \begin{bmatrix} \underline{i}_b \\ \underline{j} \end{bmatrix} = 0 \quad A \underline{i}_b = -A_j \underline{j}$$

using $Y \underline{v}_b = \underline{i}_b$: $A Y_b \underline{v}_b = -A_j \underline{j}$

KVL is written as $\underline{v} = A_a^T \underline{v}_n$

\nearrow all branch voltages \nwarrow nodal voltages

or $\begin{pmatrix} \underline{v}_b \\ \underline{v}_j \end{pmatrix} = \begin{bmatrix} A^T \\ A_j^T \end{bmatrix} \underline{v}_n \Rightarrow \begin{aligned} \underline{v}_b &= A^T \underline{v}_n \\ \underline{v}_j &= A_j^T \underline{v}_n \end{aligned}$

$\therefore A Y_b A^T \underline{v}_n = -A_j \underline{j}$

$$\begin{cases} Y \underline{v}_n = \underline{j}_n \\ Y = A Y_b A^T \\ \underline{j}_n = -A_j \underline{j} \end{cases}$$

Nodal analysis using topological formulation.

using Q : $Q_a \underline{i} = 0$ (KCL) $Q_a = [Q \quad Q_j]$

$Q \underline{i}_b = -Q_j \underline{j}$ (partition)

$Q Y_b \underline{v}_b = -Q_j \underline{j}$ (substitute constitutive relation)

$Q Y_b Q^T \underline{v}_t = -Q_j \underline{j}$ (KVL in terms of twig voltages) or independence of twig voltages

Nodal analysis in terms of twig voltages:

$$\begin{cases} Y \underline{v}_t = \underline{j}_t \\ Y = Q Y_b Q^T \\ \underline{j}_t = -Q_j \underline{j} \end{cases} \quad \underline{v} = Q_a^T \underline{v}_t \Rightarrow \begin{cases} \underline{v}_b = Q^T \underline{v}_t \\ \underline{v}_j = Q_j^T \underline{v}_t \end{cases} \quad -12-$$

For loop analysis, assume only ind. voltage sources and that every passive element has impedance type constitutive relation

$$\boxed{Z_b \underline{i}_b = \underline{v}_b}$$

$$B_a = [B_E \ ; \ B]$$

B_E part of B_a with ind. voltage sources on the twigs numbered first.

Start with KVL: $B_a \underline{v} = 0$

partition $\underline{v} = \begin{pmatrix} \underline{v}_E \\ \underline{v}_b \end{pmatrix}$

\underline{v}_b - passive branches.

$$\therefore B_E \underline{v}_E + B \underline{v}_b = 0 \Rightarrow B \underline{v}_b = -B_E \underline{v}_E$$

substitute constitutive relation:

$$B Z_b \underline{i}_b = -B_E \underline{v}_E$$

KCL: $\underline{i} = B_a^T \underline{i}_c$

("KCL" in terms of chord currents)

$$\underline{i} = \begin{pmatrix} \underline{i}_E \\ \underline{i}_b \end{pmatrix} = \begin{pmatrix} B_E^T \\ B^T \end{pmatrix} \underline{i}_c$$

or independence of chord currents)

$$\underline{i}_E = B_E^T \underline{i}_c$$

$$\underline{i}_b = B^T \underline{i}_c$$


substituting for \underline{i}_b :

$$B Z_b B^T \underline{i}_c = -B E \underline{v}_E$$

$$\left\{ \begin{array}{l} Z \underline{i}_c = \underline{e}_\ell \\ Z = B Z_b B^T \quad \text{impedance matrix} \\ \underline{e}_\ell = -B E \underline{v}_E \quad \text{loop voltages.} \end{array} \right.$$

Loop
Analysis

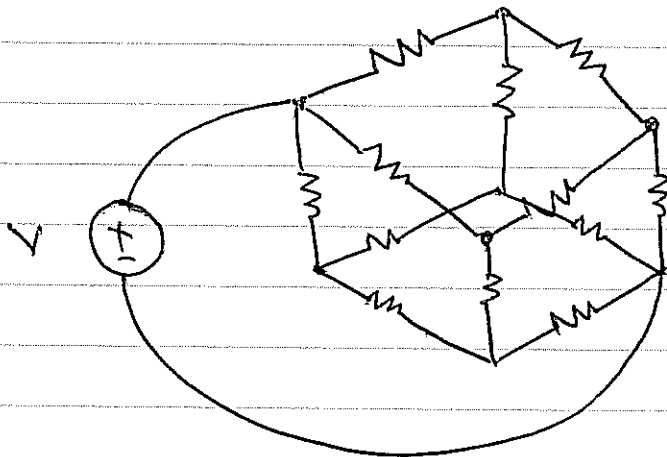Try formulating the ("all") Loop analysis for the following non-planar circuit:



All resistors have value $R = \Omega$.

Find the impedance seen by the voltage source.