


Modified Nodal Analysis (MNA)

In nodal analysis we use only nodal voltages to formulate enough equations to solve for the nodal voltages themselves.

This requires that we use "supernodes" around voltage sources and that we attempt to express controlling currents in terms of nodal voltages.

In modified nodal analysis (MNA) we keep controlling currents as variables to be solved for and we introduce auxiliary currents across voltage sources (if that branch doesn't already contain a controlling current).

Example

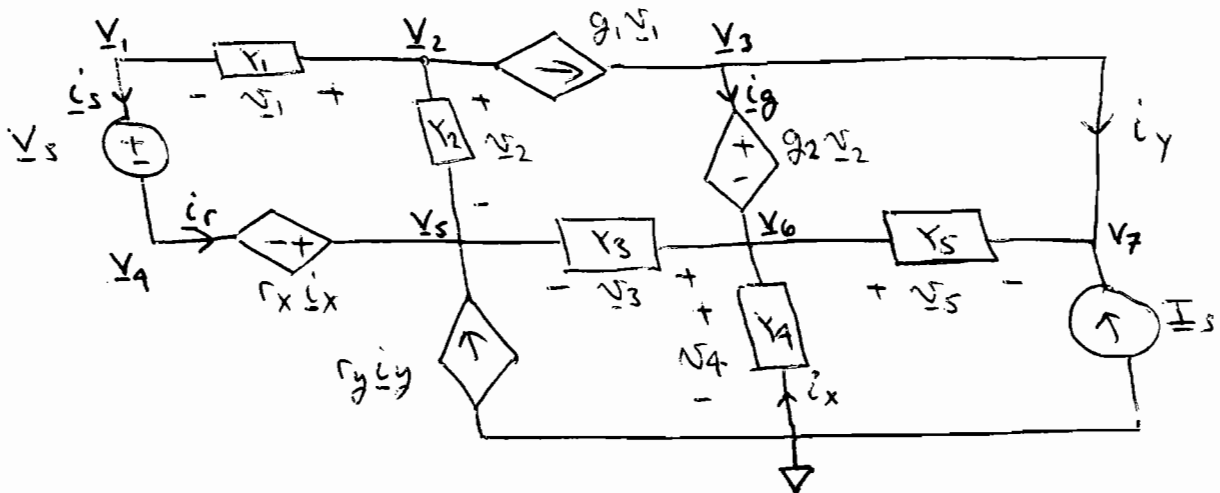

We formulate enough equations to solve for the 7 nodal voltages and the 5 auxiliary currents (2 controlling currents: i_x , i_y and 3 introduced auxiliary currents across voltage sources: i_s , i_r , i_g)

7 KCL Equations:

$$\textcircled{1} \quad Y_1 (\underline{V}_1 - \underline{V}_2) + \underline{i}_s = 0 \Rightarrow Y_1 \underline{V}_1 - Y_2 \underline{V}_2 + \underline{i}_s = 0$$

$$\textcircled{2} \quad Y_1 (\underline{V}_2 - \underline{V}_1) + Y_2 (\underline{V}_2 - \underline{V}_5) + g_1 (\underline{V}_2 - \underline{V}_1) = 0$$
$$\Rightarrow -(Y_1 + g_1) \underline{V}_1 + (Y_1 + Y_2 + g_1) \underline{V}_2 - Y_2 \underline{V}_5 = 0$$

$$\textcircled{3} \quad -g_1 (\underline{V}_2 - \underline{V}_1) + \underline{i}_y + \underline{i}_g = 0$$

$$\Rightarrow g_1 \underline{V}_1 - g_1 \underline{V}_2 + \underline{i}_y + \underline{i}_g = 0$$

$$\textcircled{4} \quad -\underline{i}_s + \underline{i}_r = 0$$

$$\textcircled{5} \quad Y_2 (\underline{V}_5 - \underline{V}_2) + Y_3 (\underline{V}_5 - \underline{V}_6) - r_y \underline{i}_y - \underline{i}_r = 0$$

$$\Rightarrow -Y_2 \underline{V}_2 + (Y_2 + Y_3) \underline{V}_5 - Y_3 \underline{V}_6 - r_y \underline{i}_y - \underline{i}_r = 0$$

$$\textcircled{6} \quad Y_3 (\underline{V}_6 - \underline{V}_5) + Y_5 (\underline{V}_6 - \underline{V}_7) - \underline{i}_x - \underline{i}_g = 0$$

$$\Rightarrow -Y_3 \underline{V}_5 + (Y_3 + Y_5) \underline{V}_6 - Y_5 \underline{V}_7 - \underline{i}_x - \underline{i}_g = 0$$

$$\textcircled{7} \quad -Y_5 \underline{V}_6 + Y_5 \underline{V}_7 - \underline{i}_y = \underline{I}_s$$

5 Aux. Eq:

$$\textcircled{8} \quad \underline{V}_1 - \underline{V}_A = \underline{V}_s$$

$$\textcircled{9} \quad -\underline{V}_A + \underline{V}_5 - r_x \underline{i}_x = 0$$

$$\textcircled{10} \quad \underline{V}_3 - \underline{V}_6 = g_2 (\underline{V}_2 - \underline{V}_5)$$

$$\Rightarrow -g_2 \underline{V}_2 + \underline{V}_3 + g_2 \underline{V}_5 - \underline{V}_6 = 0$$


$$\textcircled{11} \quad \underline{V}_3 - \underline{V}_7 = 0 \quad (\text{short circuit is equivalent to zero voltage source})$$

$$\textcircled{12} \quad Y_4 \underline{V}_6 + \underline{i}_x = 0$$

The matrix equation can now be formulated and solved on the computer.

MNA by Inspection (Using "stamps")

- the node voltages will be the initial variable that we want to solve for. (n -variables)
We know we can write n KCL equations.
- so when we write KCL at a node, all elements connected to that node which have an admittance description,
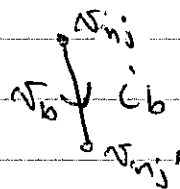
$$Y_b V_b = i_b$$


the current i_b involved in KCL can be written in terms of the node voltages:


$$Y_b (V_{n_j} - V_{n_j'}) = i_b \quad \text{KCL at node } j$$

$$Y_b (V_{n_j'} - V_{n_j}) = -i_b \quad \text{KCL at node } j'$$

\therefore in the matrix we would introduce the "stamp":

$$\begin{array}{c}
 \\
 j \\
 \\
 j' \\
 \end{array}
 \begin{bmatrix}
 & V_{n_j} & V_{n_j'} \\
 & Y_b & -Y_b \\
 & -Y_b & Y_b
 \end{bmatrix}$$

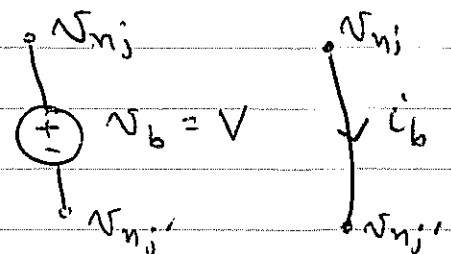
- for a voltage source when it is involved in KCL we need to use the branch current i_b , $\therefore i_b$ will be added as a variable





but if we've introduced a new variable to solve for, then we need another equation. That equation is the constitutive relation for the voltage source:

$$v_{nj} - v_{nj'} = V$$

so the stamp becomes:

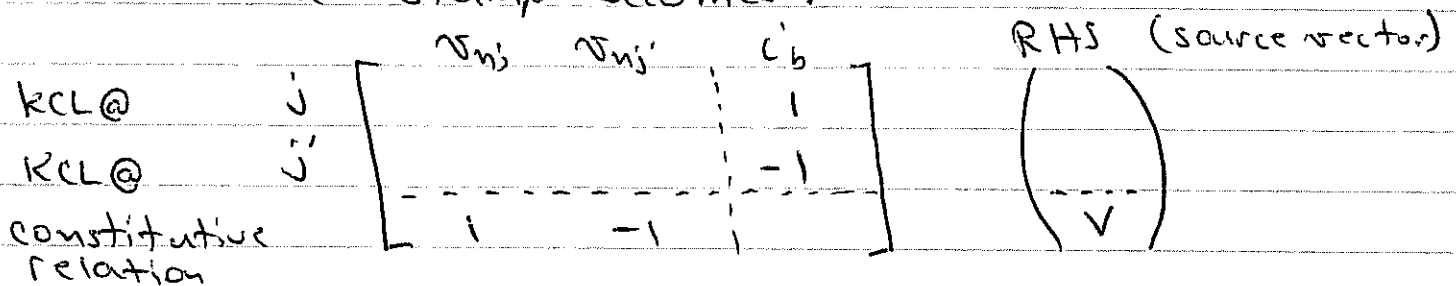

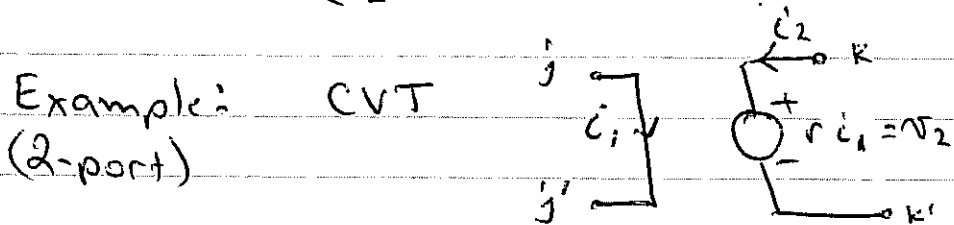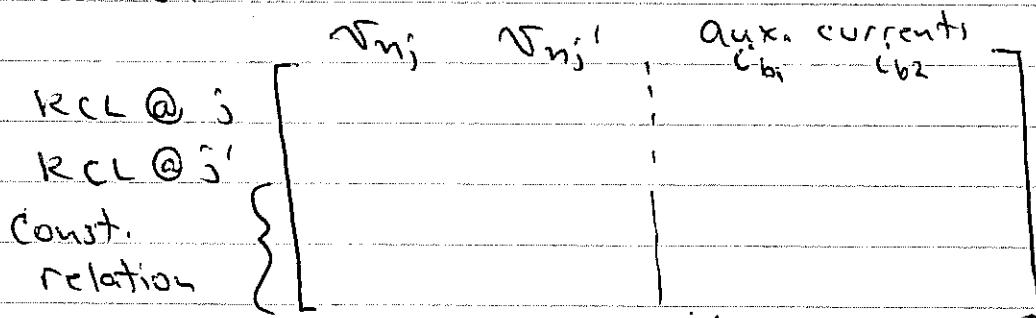The pattern for the stamps is always the same



$$v_{nj} - v_{nj'} = 0$$


$$v_{nk} - v_{nk'} - r i_1 = 0$$

$$\text{KCL @ } j : I_j = i_1$$

$$\text{KCL @ } j' : I_{j'} = -i_1$$

$$\text{KCL @ } k : I_k = i_2$$

$$\text{KCL @ } k' : I_{k'} = -i_2$$

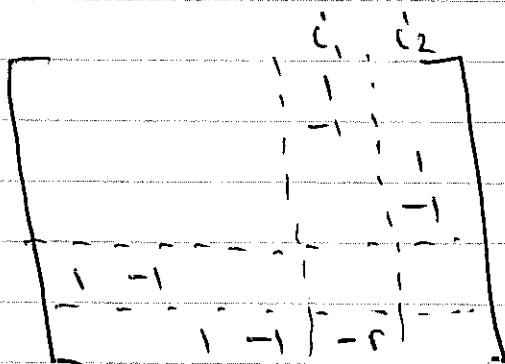

ELEMENT	SYMBOL	MATRIX	EQUATIONS
CURRENT SOURCE		$j \begin{bmatrix} -J \\ J \end{bmatrix} \\ j' \begin{bmatrix} J \\ -J \end{bmatrix}$	$I_j = J \\ I_{j'} = -J$
VOLTAGE SOURCE		$j \begin{bmatrix} V_j & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ E \end{matrix}$	$V_j - V_{j'} = E \\ I_j = I \\ I_{j'} = -I$
OPEN CIRCUIT		—	$V = V_j - V_{j'}$
SHORT CIRCUIT		$j \begin{bmatrix} V_j & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \end{matrix}$	$V_j - V_{j'} = 0 \\ I_j = I \\ I_{j'} = -I$
ADMITTANCE		$j \begin{bmatrix} y & V_j \\ j' & \begin{bmatrix} -y \\ y \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \end{matrix}$	$I_j = y(V_j - V_{j'}) \\ I_{j'} = -y(V_j - V_{j'})$
IMPEDANCE		$j \begin{bmatrix} V_j & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ -I \end{matrix}$	$V_j - V_{j'} - zI = 0 \\ I_j = -I_{j'} = I$
NULLATOR		$j \begin{bmatrix} V_j & V_{j'} \\ j' & \begin{bmatrix} 1 & -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \end{matrix}$	$V_j - V_{j'} = 0 \\ I_j = I_{j'} = 0$
NORATOR		$j \begin{bmatrix} I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \end{matrix}$	$V, I \text{ ARE ARBITRARY}$
VCT		$j \begin{bmatrix} V_j & V_{j'} \\ k & \begin{bmatrix} g & -g \\ -g & g \end{bmatrix} \\ k' & \begin{bmatrix} -g \\ g \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \end{matrix}$	$I_j = 0 \\ I_{j'} = 0 \\ I_k = g(V_j - V_{j'}) \\ I_{k'} = -g(V_j - V_{j'})$


Fig. 4.4.1. Ideal elements in the modified nodal formulation without graphs.

ELEMENT	SYMBOL	MATRIX	EQUATIONS
VVT		$j \begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ k & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ k' & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} -\mu & 1 & -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \\ I \\ I \\ I \end{matrix}$	$-\mu V_j + \mu V_{j'} + V_k \\ -V_{k'} = 0 \\ I_k = 1 \\ I_{k'} = -I$
CCT		$j \begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ k & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ k' & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 & -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \\ \sigma I \\ -\sigma I \end{matrix}$	$V_j - V_{j'} = 0 \\ I_j = -I_{j'} = I \\ I_k = -I_{k'} = \sigma I$
CVT		$j \begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I_1 & I_2 \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ k & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ k' & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 & -1 \end{bmatrix} \\ m+2 & \begin{bmatrix} 1 & -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I_1 \\ I_1 \\ I_2 \\ -I_2 \end{matrix}$	$V_j - V_{j'} = 0 \\ V_k - V_{k'} - r I_1 = 0 \\ I_j = -I_{j'} = I_1 \\ I_k = -I_{k'} = I_2$
OPERATIONAL AMPLIFIER		$j \begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 & -1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \\ I \\ -I \end{matrix}$	$V_j - V_{j'} = 0 \\ I_k = -I_{k'} = I$
CONVERTOR		$j \begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ k & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ k' & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 & -1 & -K_1 & K_1 \end{bmatrix} \end{bmatrix} \begin{matrix} I \\ I \\ -K_2 I \\ K_2 I \end{matrix}$	$V_j - V_{j'} - K_1 V_k + K_1 V_{k'} = 0 \\ I_j = -I_{j'} = I \\ I_k = -I_{k'} = -K_2 I$ FOR IDEAL TRANSFORMER $K_1 = K_2 = n$
TRANSFORMER		$j \begin{bmatrix} V_j & V_{j'} & V_k & V_{k'} & I_1 & I_2 \\ j' & \begin{bmatrix} 1 & 1 \\ -1 & -1 \end{bmatrix} \\ k & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ k' & \begin{bmatrix} 1 \\ -1 \end{bmatrix} \\ m+1 & \begin{bmatrix} 1 & -1 \end{bmatrix} \\ m+2 & \begin{bmatrix} -sL_1 & -sM \\ -sM & -sL_2 \end{bmatrix} \end{bmatrix} \begin{matrix} I_1 \\ I_1 \\ I_2 \\ -I_2 \end{matrix}$	$V_j - V_{j'} - sL_1 I_1 - sM I_2 = 0 \\ V_k - V_{k'} - sM I_1 - sL_2 I_2 = 0 \\ I_j = -I_{j'} = I_1 \\ I_k = -I_{k'} = I_2$

Fig. 4.4.1. (Continued)


Let's redo the previous example using the stamps in Fig. 4.4.1.

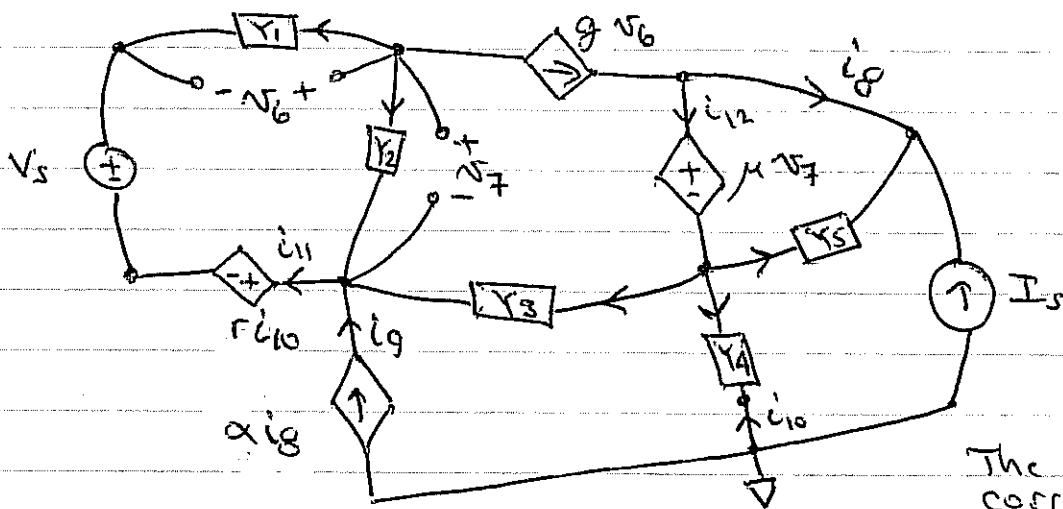First we should redraw the network so that all branches for the two-ports are clearly identifiable.



Note that i_{10} was added on one side of CVT v_6 as one side of VCT and v_7 as one side of VVT.

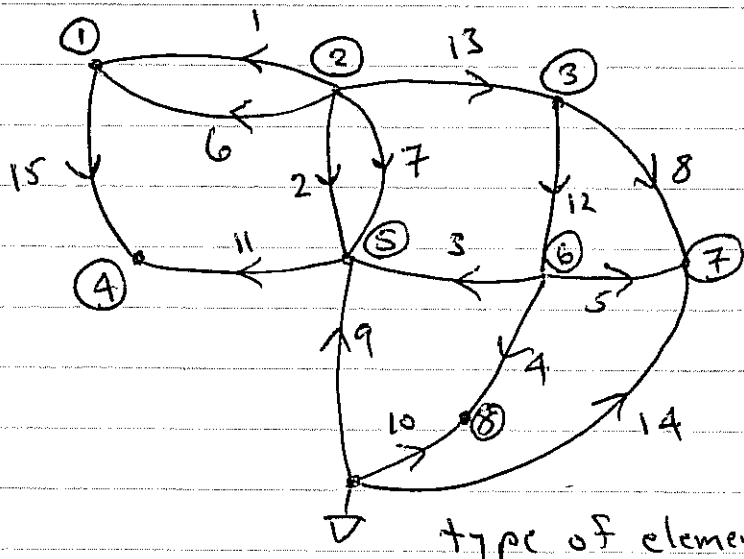The CCT was already correctly represented.



In MNA, it is the nodal voltages which are solved for. So there was no need to number the branches.

The information can be written as a list of elements, the type of element, the nodes at the terminals j, j' for one ports, j, j', k, k' for two ports, and the appropriate parameters which define the constitutive relations for that element.

Let's assume that branches 1 and 2 are given as admittances G_1 and sC_2 while branches 3, 4, and 5 are impedances R_3, R_4, sL_5 .

Type	Nodes	Parameters
G	2 1	G_1
C	2 5	C_2 entered as sC_2 or $j\omega C_2$
R	6 5	R_3 adds i_{65}
R	6 8	R_4 adds i_{68}
L	6 7	L_5 adds i_{67} and entered as $-sL_5$ or $-j\omega L_5$
VCT	2 1 2 3	g no aux. current
VVT	2 5 3 6	A aux. current i_{36}
CCT	3 7 0 5	α aux. currents i_{37}
CVT	0 8 5 4	r aux. currents i_{08}, i_{54}
CS	0 7	I_s RHS
VS	1 4	V_s aux. current i_{14} and RHS

We will have 8 nodal variables and 8 auxiliary variables in our MMA equation.

The CVT adds two auxiliary currents

The CCT and VVT both add one

The VS adds one

Each of the impedance variables adds one auxiliary current

The final matrix equation will look like $T\underline{x} = \underline{w}$

$$T \text{ is } 16 \times 16 \quad \underline{x} = \begin{pmatrix} \underline{v_n} \\ \underline{i_a} \end{pmatrix} \quad \underline{v_n} \text{ is } 8 \times 1 \quad \underline{w} = 16 \times 1$$

$$(T = G + SC) \quad \underline{i_a} \text{ is } 8 \times 1$$

For the auxiliary currents we can name them as per the nodes they fall between:

$$\underline{i_a} = \begin{pmatrix} i_{65} & 9 \\ i_{68} & 10 \\ i_{67} & 11 \\ i_{36} & 12 \\ i_{37} & 13 \\ i_{08} & 14 \\ i_{54} & 15 \\ i_{14} & 16 \end{pmatrix} \quad \underline{v} = \begin{pmatrix} v_{n1} \\ v_{n2} \\ v_{n3} \\ v_{n4} \\ v_{n5} \\ v_{n6} \\ v_{n7} \\ v_{n8} \end{pmatrix}$$

$$G \quad 2 \quad 1 \quad G_1 \quad \begin{matrix} 2 & 1 \\ \begin{bmatrix} G_1 & -G_1 \\ -G_1 & G_1 \end{bmatrix} \end{matrix}$$

$$C \quad 2 \quad 5 \quad C_2 \quad \begin{matrix} 2 & 5 \\ \begin{bmatrix} SC_2 & -SC_2 \\ -SC_2 & SC_2 \end{bmatrix} \end{matrix}$$

$$R \quad 6 \quad 5 \quad R_3 \quad \begin{matrix} 6 & 5 & 9 \\ \begin{bmatrix} & & 1 \\ & & -1 \\ 1 & -1 & -R_3 \end{bmatrix} \end{matrix}$$

$$R \quad 6 \quad 8 \quad R_4 \quad \begin{matrix} 6 & 8 & 10 \\ \begin{bmatrix} & & 1 \\ & & -1 \\ 1 & -1 & -R_4 \end{bmatrix} \end{matrix}$$

