

ECE 220

---

**introduction to *spice* source files**

## The Input (\*.cir) File

In `pspice`, this file must be named `<filename>.cir`. The source file for any version of `spice` has the following format.

```
TITLE
ELEMENT DESCRIPTIONS
.MODEL STATEMENTS
ANALYSIS COMMANDS
OUTPUT COMMANDS
.END
```

### Important points:

- The first line of this file is used as a title on output files. It is not included in the circuit description. A common and frustrating error is caused by omitting the title.
- The file must end with the command `.END` followed by a newline.
- Comment entire lines by beginning them with `'*` or the rest of a line by using a `;`
- Continue a statement on a new line with `'+`

## The Circuit Description

A circuit description in `spice`, which is frequently called a **netlist**, consists of a statement defining each circuit element.

Connections are described by naming nodes. (The usual names are actually numbers.) One node name has a defined meaning. **Node 0 is ground!**

The format of an element description is


```
<letter><name> <n1> <n2> ...[mname] [parvals]
```

where `<...>` must be present and `[...]` is optional.

- `<letter>` is a single letter denoting the component type
- `<name>` is a unique alpha-num combination describing the particular instance of this component
- `<ni>` is the name of a node
- `[mname]` is the (optional) model name
- `[parvals]` are (sometimes optional) parameter values
 
## Sign Conventions

Two-terminal elements (including sources!) assume the “load” sign convention



The power  $P = IV$  associated with an element is positive when the element **absorbs** power.

*spice* shows sources delivering negative power.

## Passive Elements

The `<letter>` that begins an element instance denotes the circuit element. The passive elements are

R or `r` for resistors, L or `l` for inductors, and C or `c` for capacitors.

This `<letter>` is followed by a unique instance name and then (in order) the nodes associated with + and - voltage and the value of the associated parameter ( $R$ ,  $L$ , or  $C$ ).

### Examples:

- `R1 5 0 20k`
- `cload nIN GND 250pF`
- `L4 122 21 4mH`

## Powers of Ten

The following abbreviations for powers of ten are recognized by `spice`.

F	P	N	U	M	K	MEG	G	T	MIL
femto	pico	nano	micro	milli	kilo	mega	giga	tera	mil ( $10^{-3}$ inch)
$10^{-15}$	$10^{-12}$	$10^{-9}$	$10^{-6}$	$10^{-3}$	$10^{+3}$	$10^{+6}$	$10^{+9}$	$10^{+12}$	$25.4 \times 10^{-6}$

Once a valid suffix is read, `spice` ignores following letters. Thus `10pF`, `10pAmps`, and `10psec` all simply represent the value  $10^{-12}$ .

`MIL` is used to convert distances in thousands of an inch, since `spice` uses metric lengths.

## Independent Sources

`V<name> <n+> <n-> [type] <val>`

defines an independent voltage source with its + terminal at node `n+` and its - node at node `n-`.

`I<name> <n+> <n-> [type] <val>`

defines an independent current source whose current flows through the source from node `n+` to node `n-`.

### Examples:

- `Vdd 4 0 5` defines a 5 V source with the + terminal connected at node 4 and the - terminal connected at node 0 (ground)
- `ibias 18 4 DC 15m`
- `V2 3 0 25V` (`spice` recognizes the common abbreviations for units, which helps to make source files more easily understood by humans.)

The optional `type` argument will be described in the analysis commands.

## Voltage-Controlled Dependent Sources

The voltage-controlled dependent sources are defined using statements of the form

```
<letter><name> <nout+> <nout-> <nc+> <nc-> <gain>
```

or

```
<letter><name> <nout+> <nout-> (<nc+>,<nc->) <gain>
```

where  $E$  is a voltage-controlled voltage source,  $G$  is a voltage-controlled current source, the output voltage is connected between nodes  $nout+$  and  $nout-$ , and the control voltage is measured at node  $nc+$  with respect to node  $nc-$ .

### Examples:

- `Ex 5 1 4 3 10` defines a voltage source that makes node 5 a voltage  $10(v_4 - v_3)$  above the voltage at node 1
- `G1 2 1 (5,8) 50m` defines a current source connected between node 2 (the + node) and node 1 and supplying a current  $50m\mathcal{U}(v_5 - v_8)$



## Current-Controlled Dependent Sources

The current-controlled dependent sources are defined by statements of the form

```
<letter><name> <nout+> <nout-> <vcontrol> <gain>
```

where F is a current-controlled current source, H is a current-controlled voltage source, and the output current source is connected between nodes `nout+` and `nout-`, with positive current flowing through the source from node `nout+` to `nout-`. The control current flows from the positive node of the source `vcontrol` through the source and out the negative node.

### Examples:

- `Fds 11 9 Vsens 1.25` defines a current source connected from node 11 to node 9 that generates a current 1.25 times the current flowing through the source `Vsens`.
- `H1 30 20 v5 100k` defines a voltage source connected from node 30 to node 20 and supplying a voltage  $100\text{ k}\Omega$  times the current through the source `v5`.


**It is frequently necessary to add a voltage source with value 0 V to the circuit to sense the control current for these sources!**

## Diodes

Diodes are defined using two statements. The netlist definition is of the form

$$D\langle\text{name}\rangle \langle n+\rangle \langle n-\rangle \langle\text{model-name}\rangle$$

 **Example:** `D1 4 2 my-diode` corresponds to



The  $\langle\text{model-name}\rangle$  must be defined using a `.MODEL` statement

$$.MODEL \langle\text{model-name}\rangle D ( [\text{parameter} = \text{value}] \dots )$$

Continuing the above example,

$$.MODEL \text{my-diode} D ( IS=1.4e-18 N=1.2 )$$

where  $IS$  is the saturation current and  $N$  is the ideality factor (sometimes called the emission coefficient). There are approximately 30 parameters which can be specified for diodes. Those not explicitly specified have default values.

## Useful Diode Model parameters

Parameter	Description	Units	Default
IS	Reverse saturation current	Amp	$10^{-14}$
XTI	Temperature exponent of IS		3
N	Ideality factor (emission coefficient)		1
BV	Reverse breakdown "knee" voltage	Volt	$\infty$
RS	Parasitic series resistance	Ohm	0
CJO	Zero-bias junction capacitance	Farad	0


## Bipolar Junction Transistors

The BJT also requires both a netlist statement and a `.MODEL`. A BJT is included in the netlist with a statement of the form

```
Q<name> <nc> <nb> <ne> <model-name>
```

where the collector is connected at node `nc`, the base at node `nb`, and the emitter at node `ne`.

 **Example:** `Q3 6 3 0 my-npn` corresponds to



The `model-name` is defined as

```
.MODEL <model-name> <nnp | pnp> ( [parameter = value] ... )
```

Continuing the example,

```
.MODEL my-npn npn ( BF = 175 IS=1e-17 VA=75 BR=2 )
```

where  $BF$  is the forward  $\beta$ ,  $IS$  is the saturation current,  $VA$  is the Early voltage, and  $BR$  is the reverse  $\beta$ . There are approximately 60 parameters for BJTs.


## MOSFETs

The BJT again requires both a netlist statement and a `.MODEL`. A MOSFET is included in the netlist with a statement of the form

```
M<name> <nd> <ng> <ns> <nb> <model-name> [L=value] [W=value]
```

where the drain, gate, source, and body are connected at nodes `nd`, `ng`, `ns`, and `nb` respectively. The length `L` and width `W` are optional.

 **Example:** `Md 4 3 2 10 my-pmos L=1.5u W=4u` corresponds to



The `model-name` is defined as

```
.MODEL <model-name> <nmos | pmos> ( [parameter = value] ... )
```

Continuing the example,

```
.MODEL my-pmos pmos ( VTO=-0.8V KP=5e-4 LAMBDA=0.01 )
```

where `VTO` is the threshold voltage, `KP` is the transconductance parameter, and `LAMBDA` is the channel-length modulation coefficient.

## Subcircuits



A subcircuit simplifies *spice* netlists by allowing re-use of a set of circuit elements. The syntax is

```
SUBCKT <SubName> <N1> <N2> ...  
  
...  
  
.ENDS
```

The *SubName* is the name used to reference the subcircuit, and the nodes are the internal node numbers used to connect to the subcircuit.

A subcircuit can contain any *spice* netlist statements, including `.model` statements and other subcircuits.

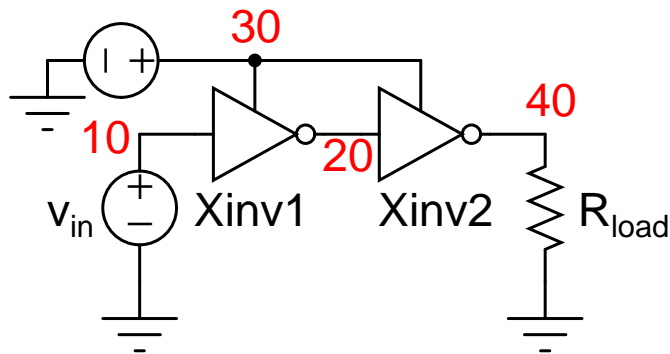 Any elements, nodes, models, subcircuits, or definitions in the subcircuit are completely local to the subcircuit.



```
* subcircuit example
```

```
.subckt inverter 1 2 3
```

```
*          input | |
```

```
*          output |
```

```
*          dc supply
```

```
mp 2 1 3 3 mypmos
```

```
mn 2 1 0 0 mynmos
```

```
.model mypmos pmos( ... )
```

```
.model mynmos nmos( ... )
```

```
.ends
```

```
Vdd 30 0 dc 3.6V
```

```
vin 10 0 dc 0V
```

```
Xinv1 10 20 30 inverter
```

```
Xinv2 20 40 30 inverter
```

```
Rload 40 0 100k
```

```
.dc vin 0 3.6 0.1
```

```
.end
```

## **.AC Small-Signal Analysis**

.AC calculates the small-signal response as a function of frequency. The command is

```
.AC <type> <npts> <f-start> <f-end>
```

where <type> is one of

**LIN** (linear sweep) The analysis is repeated at <npts> linearly-spaced frequencies starting at <f-start> and ending at <f-end>.

**DEC** (log sweep by decades) The analysis is repeated at frequencies starting with <f-start> and ending with <f-end>. The frequencies are equally-spaced on a  $\log_{10}$  scale with <npts> per decade.


**OCT** (log sweep by octaves) The analysis frequencies start at <f-start> and end with <f-end>, with <npts> points per octave.

A source whose frequency is swept has a `type` designation `AC` included in its element description.



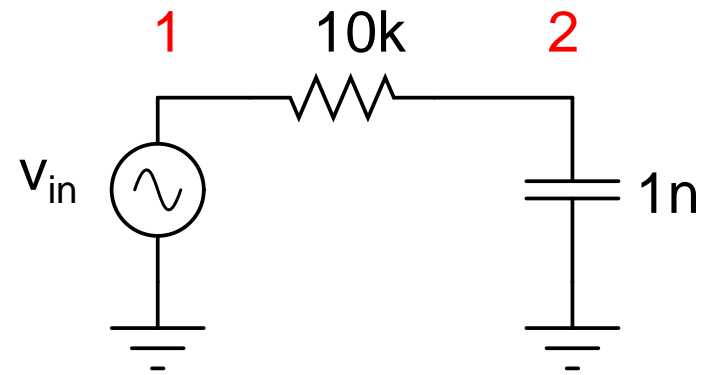**. AC Example**

```
RC circuit
r1 1 2 10k
c1 2 0 1n
vin 1 0 ac 1 dc 0
.ac dec 10 .01 10
.probe
.end
```



## .DC Sweep

.DC calculates the DC voltages and currents in a circuit for a range of values of a chosen variable or variables. The .DC command has three forms.

.DC [LIN] <var1> <s1> <e1> <d1> [<var2> <s2> <e2> <d2>]  
sweeps `var1` from `s1` to `e1` with a linear increment `d1`. If the second set of values is present, the entire first analysis will be done for each value of `var2`.


.DC <DEC | OCT>] <var1> <s1> <e1> <np1> [<var2> ...]  
does a log sweep, adjusting `var1` from `s1` to `e1` in decades (DEC) or octaves (OCT) with `np1` points per interval. If the second set of values is present, the entire first analysis will be done for each value of `var2`.

.DC <var1> LIST <val1> <val2> [...] [<var2> ...]  
performs the analysis for a list of values. Again, the entire first analysis is performed for every value in the second list.

A source whose value is used in a .DC sweep has a `type` designation DC included in its element description.

 **.DC Example**

```
1 transistor inverter
vbias 3 0 5V
vs 1 0 dc 0V
rb 1 2 20k
rc 3 4 2k
q 4 2 0 gennpn
...
.dc vs 0 5 0.05
...
.end
```




## .TF - Transfer Function

```
.TF <var-out> <source-in>
```

calculates the small-signal gain from `source-in` to `var-out`, as well as the input and output resistances. If `var-out` is a current, it must be the current through a voltage source. (You may have to add a  $0V$  source to sense this current.)
 
### Example:

```
tf example
vin 1 0 dc 0.5Vac 0.1V
rin 1 2 5k
ro 2 0 10k
...
tf v(2) vin
...
.end
```



## `.TRAN - Transient Analysis`

`.TRAN` calculates the voltages and currents in a circuit as a function of time. The form of the command is

```
.TRAN[/OP] <print-inc> <t-end> [print-start] [UIC]
```

The operating point for the conditions at the start of the transient analysis is calculated, but will not be displayed unless the optional `.TRAN/OP` version of the command is used.

`print-inc` is the time step for the output (**not** the time step for the calculation!), and `t-end` is the end of the simulation time period.

The optional argument `print-start` only reports results after that time, and `UIC` indicates that the simulation should use initial conditions. (Initial conditions are set either with a `.IC` command or by following the element definition of a capacitor with `IC=<voltage>` and that for an inductor with `IC=<current>`).

## Input Sources for .TRAN

The source types available include EXP for exponential waveforms, PULSE, PWL for piecewise-linear waveforms, and SIN.

```
EXP( <v1> <v2> [Td1 [Tau1 [Td2 [Tau2]]]])
```

defines an exponential pulse which has an initial value of  $v1$ , starts at time  $Td1$ , rises with a time constant  $Tau1$  until time  $Td2$ , then falls with a time constant  $Tau2$ .

```
PULSE( <v1> <v2> [Td [Tr [Tf [pw [tau]]]])
```

represents a pulse train with low voltage  $v1$  and high voltage  $v2$ . The first pulse starts at time  $T1$ , has rise time  $Tr$  and fall time  $Tf$ , holds  $v2$  for a time  $pw$ , and has a period  $tau$ .

```
PWL ( <t1> <v1> [t2 v2 [t3 v3 ...]] )
```


describes a piecewise-linear waveform with each  $t$   $v$  defining a “corner.”

```
SIN ( <v0> <va> [f [Td [df [phi]]]])
```

defines an exponentially-damped sine waveform with peak amplitude  $va$ , frequency  $f$ , damping factor  $df$ , and phase  $phi$  in degrees. The waveform has the offset voltage  $v0$ , and holds that value for a time  $Td$  before the time-dependence begins.
 
## .TRAN Example

```
tran example
vin 1 0 pulse(0V 5V 0 0.1n 0.1n
+ 1u 2u)
vcontrol 2 0 dc 5V
mpass 1 2 3 0 mynmos L=5u W=5u
cl 3 0 10p
...
.model mynmos nmos(kp=0.01m
+ vto=0.8)
...
.tran 0.1u 2.5u
...
.end
```



## **.OP - Operating Point**

The `.OP` command writes detailed information about the default dc operating point to be written in the `*.out` file. (This information is actually calculated by `spice`.)

The current and power of all voltage sources is given, as well as the small-signal model parameters for all semiconductor devices.

The `.TRAN/OP` command supplies operating point information for the bias point of a transient analysis.



## Writing results to a file

The results of an analysis request can be written to a file using the `.PRINT` command. The form of the command is

```
.PRINT <type> <OV1> <OV2> <OV3> ...
```

The output variables are `OV1`, `OV2`, .... Node voltages and branch currents can be specified as magnitude (M), phase (P), real (R), or imaginary (I) by adding the appropriate suffix to V or I using the following designations:

**M:** Magnitude

**DB:** Magnitude in dB

**P:** Phase

**R:** Real part

**I:** Imaginary part

**Example:** `.print dc vm(4,0) vdb(4,2) ip(3,2)`